


Ohm's Law

$$V \propto I$$

$$\tan\theta = \frac{dV}{dI}$$

$$V = RI$$

R = Resistance

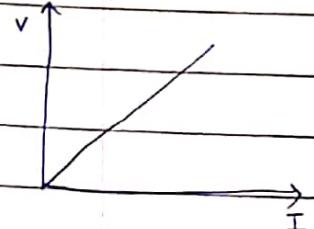

$$V_d = \mu E$$

$$I = nqAV_d$$

$$= nqA\mu E$$

$$= nqA\mu \frac{V}{l}$$

$$\frac{V_A - V_B}{R}$$

$$I = \frac{V_A - V_B}{R}$$

$$\frac{V}{I} = \left(\frac{1}{nq\mu} \right) \frac{l}{A} = R$$

$$R = \frac{\rho l}{A}$$

$$\rho = \frac{1}{nq\mu} = \text{resistivity}$$

For ohm's law -

l = same

A = same

T = Temp.

Kirchoff's Laws

Kirchoff's Current Law (KCL) -

$$\sum I = 0$$

$I_{\text{entering}} = I_{\text{leaving}}$ at a node


When two passive elements are connected and there is a division of current then it is node.

Path connecting 2 nodes is a branch.

$$n = 3 \quad b = 5 \quad l = 3$$

$$b = l + n - 1$$

$$5 = 3 + 3 - 1$$

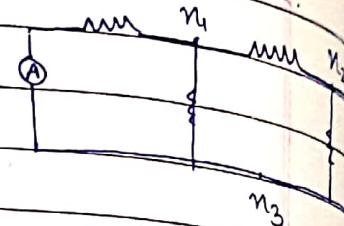

Kirchhoff's Voltage Law

Summation of voltage drop across the circuit is equal to zero.

Passive Components

i) Inductor (L) - Unit is Henry

$$V = L \frac{di}{dt}$$

$$i = \frac{1}{L} \int_0^t V dt$$


$$P = V \times I$$

$$\frac{dw}{dt} = Li \frac{di}{dt}$$

$$dw = Li di$$

$$W = \frac{1}{2} LI^2$$

D. Calculate P & W?

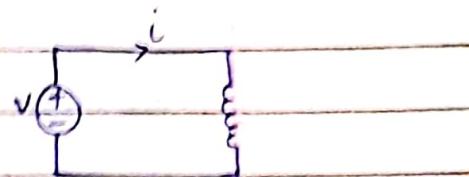


$$\text{Ans. } i = 10e^{-5t} \text{ A}$$

$$V = e^{-5t}(1 - 5t) \text{ V}$$

$$P = 10t e^{-10t} - 50t^2 e^{-10t}$$

$$W = 5t^2 e^{-10t}$$

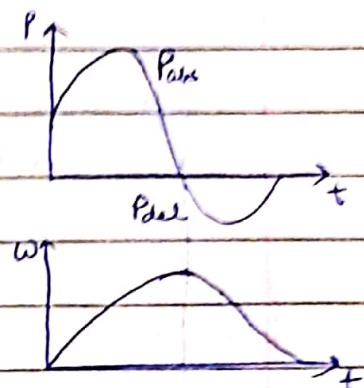

Conclusion -

- 1) Inductor opposes instantaneous change in current.
- 2) Inductor only works with A.C. current. It will short-circuit with D.C. current.
- 3) Inductor does not dissipate energy as heat. It stores energy and then delivers it.

2) Capacitor (C) - Unit is Farad

$$i = \frac{cdv}{dt}$$

$$V = \frac{1}{C} \int idt$$

$$P = V \times I$$

$$\frac{dw}{dt} = V \times \frac{1}{C} C \frac{dv}{dt}$$

$$dw = C V dv$$

$$W = \frac{1}{2} C V^2$$

Conclusion

- 1) Acts as open circuit to D.C. current
- 2) Opposes sudden change in voltage.
- 3) Does not dissipate energy.


Voltage Division

$$V_1 = IR_1$$

$$V_2 = IR_2$$

$$V = V_1 + V_2 = I(R_1 + R_2)$$

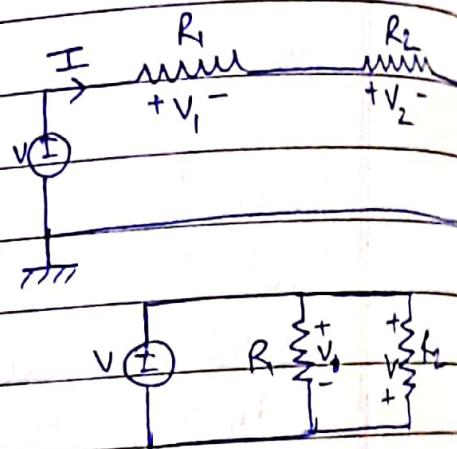
$$\frac{1}{R} = \frac{1}{R_1} + \frac{1}{R_2}$$





Current Division

$$I_1 = \frac{IR_2}{I_1 + I_2}$$

$$I_2 = \frac{IR_1}{I_1 + I_2}$$

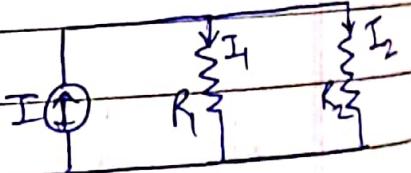

Delta to Y Conversion

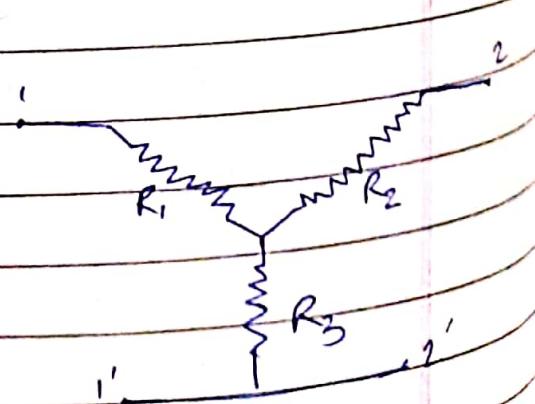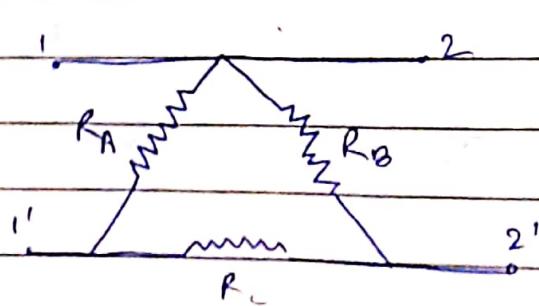

$$R_{11'} = Ra/(R_b + R_c)$$

$$R_{22'} = Rb/(R_a + R_c)$$

$$R_{12} = Rc/(R_a + R_b)$$

$$R_{11'} = R_1 + R_3$$

$$R_{22'} = R_2 + R_3$$

$$R_{12} = R_1 + R_2$$

$$R_1 + R_3 = R_a / (R_b + R_c) - \textcircled{1}$$

$$R_2 + R_3 = R_b / (R_a + R_c) - \textcircled{2}$$

$$R_1 + R_2 = R_c / (R_a + R_b) - \textcircled{3}$$

$$\textcircled{2} - \textcircled{1}$$

$$R_1 - R_2 = R_a / (R_b + R_c) - R_b / (R_a + R_c) - \textcircled{4}$$


$$\textcircled{3} + \textcircled{4}$$

$$2R_1 = R_c / (R_a + R_b) + R_a / (R_b + R_c) - R_b / (R_a + R_c)$$

$$= \frac{R_c (R_a + R_b)}{R_a + R_b + R_c} + \frac{R_a (R_b + R_c)}{R_a + R_b + R_c} - \frac{R_b (R_a + R_c)}{R_a + R_b + R_c}$$

$$2R_1 = \frac{R_c R_a + R_c R_b + R_a R_b + R_a R_c - R_a R_b - R_b R_c}{R_a + R_b + R_c}$$
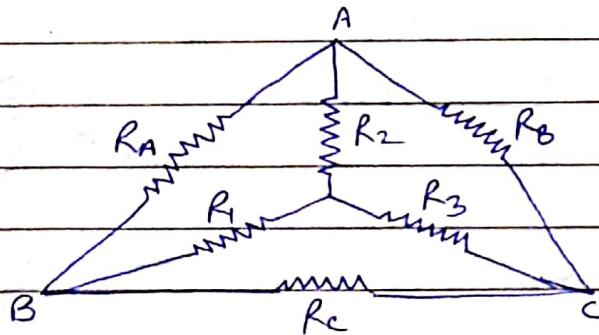
$$R_1 = \frac{R_a R_c}{R_a + R_b + R_c}$$



$$R_1 = \frac{R_a R_c}{R_a + R_b + R_c}$$

$$R_2 = \frac{R_a R_b}{R_a + R_b + R_c}$$

$$R_3 = \frac{R_b R_c}{R_a + R_b + R_c}$$



$$\textcircled{1} \quad \frac{R_1}{R_2} = \frac{R_c}{R_b} \quad \textcircled{2} \quad R_2 = \frac{R_a}{R_c} \quad \textcircled{3} \quad R_1 = \frac{R_a}{R_3} \frac{R_c}{R_b}$$

$$\textcircled{4} \quad R_1 R_2 = \frac{R_a^2 R_b R_c}{(R_a + R_b + R_c)^2} \quad \textcircled{5} \quad R_2 R_3 = \frac{R_a R_b^2 R_c}{(R_a + R_b + R_c)^2}$$

$$\textcircled{6} \quad R_3 R_1 = \frac{R_a R_b R_c^2}{(R_a + R_b + R_c)^2}$$

$$R_1 R_2 + R_2 R_3 + R_3 R_1 = \frac{R_a R_b R_c}{R_a + R_b + R_c} - \textcircled{7}$$
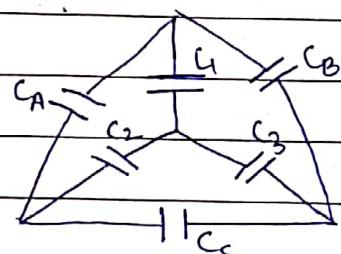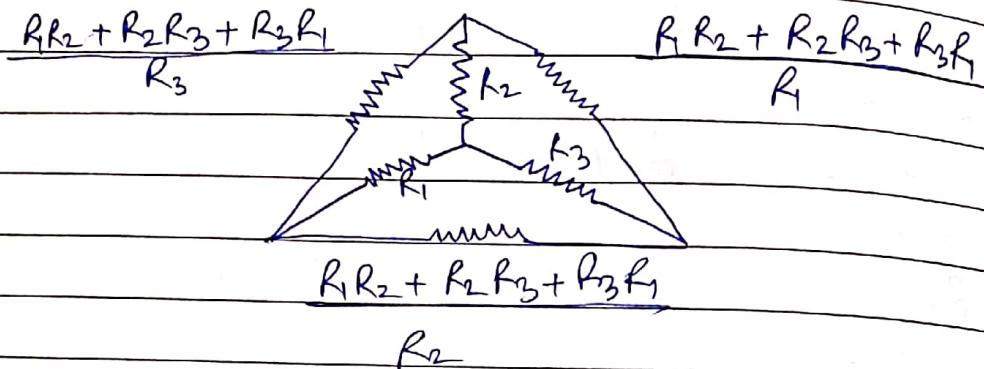
$$R_b = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_1}$$





$$\frac{1}{C_1} = \frac{1}{W C_A} \times \frac{1}{W C_B}$$

$$\frac{1}{W C_A} + \frac{1}{W C_B} + \frac{1}{W C_C}$$

$$\frac{1}{C_1} = \frac{C_c}{C_B C_c + C_A C_c + C_A C_B}$$

$$C_1 = \frac{C_B C_c + C_A C_c + C_A C_B}{C_c}$$



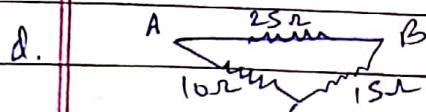
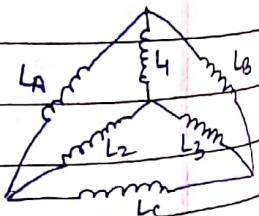
$$C_1 = \frac{L_A L_B}{L_A + L_B + L_C}$$



$$\text{Ans. } \frac{250}{25+10+15} = 5\Omega$$

$$\frac{\frac{25}{25+10+15} \times \frac{15}{25+10+15}}{\frac{25}{25+10+15} + \frac{15}{25+10+15}} = 7.5\Omega$$

$$\frac{15}{25+10+15} = 3\Omega$$

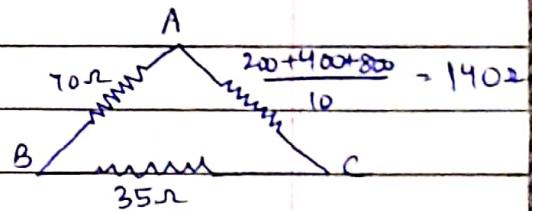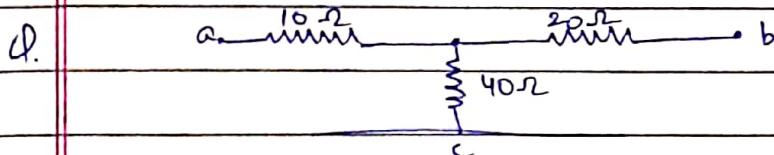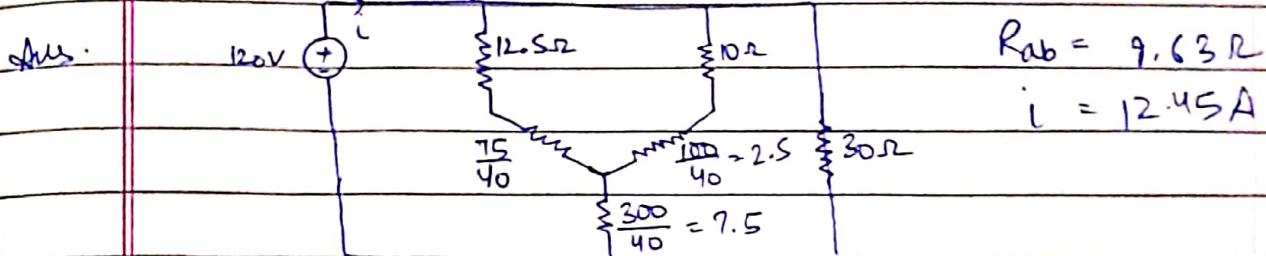
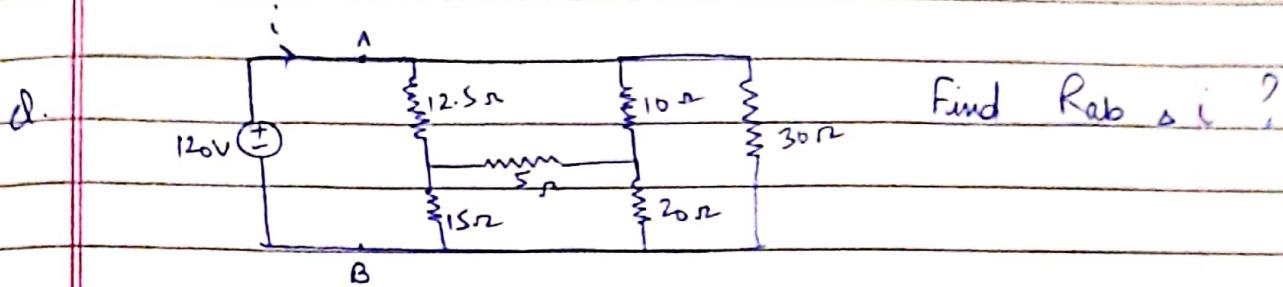


Nodal Analysis

→ Based on KCL

→ Node variable

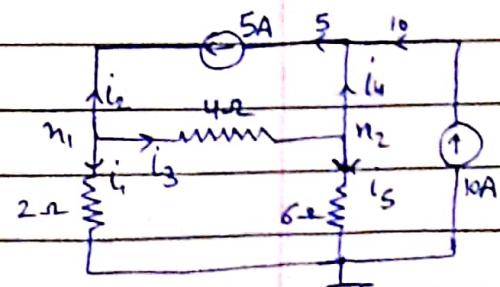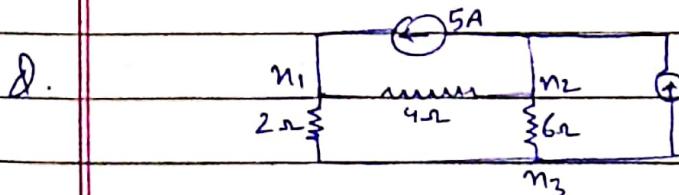→ Among all one will be reference node and others will be variable ($V_1, V_2, V_3, \dots, V_{n-1}$)



Ans. let $V_{n_3} = 0$

At node n_1 ,

$$i_1 + i_2 + i_3 = 0$$

$$\frac{V_1 - 0}{2} + \left(-\frac{5}{4}\right) + \frac{V_1 - V_2}{6} = 0$$

$$V_1 - 5 + V_1 - 14 = 0$$

$$\frac{3}{4}V_1 - \frac{V_2}{4} = 5$$

$$3V_1 - V_2 = 20 \quad \text{---(1)}$$

At node n_2

$$i_4 + i_5 = i_3$$

$$\frac{5}{6}(-10) + \frac{V_2 - 0}{4} = \frac{V_1 - V_2}{4}$$

$$\frac{V_2}{6} - \frac{V_1}{4} + \frac{V_2}{4} = 10 - 5$$

$$\frac{5}{12}V_2 - \frac{V_1}{4} = 10 - 5$$


$$5V_2 - 3V_1 = 160 \quad \text{---(2)}$$

$$(2) + (1)$$

$$5V_2 - 3V_1 = 60$$

$$+ 3V_1 - V_2 = 20$$
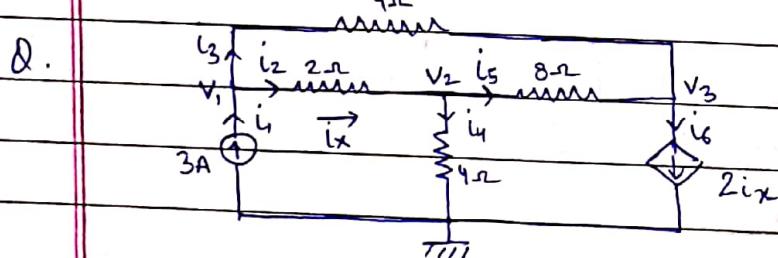
$$4V_2 = 80 \Rightarrow V_2 = 20V, V_1 = \frac{40V}{3}$$



Aus. At node n_1 ,

$$i_1 + i_2 + i_3 = 0$$

$$-3 + \frac{V_1 - V_2}{2} + \frac{V_1 - V_3}{4} = 0 \quad \text{---(1)}$$

At node n_2 ,

$$i_4 + i_5 - i_2 = 0$$

$$\frac{V_2}{4} + \frac{V_2 - V_3}{8} - \frac{V_1 - V_2}{2} = 0 \quad \text{---(2)}$$

At node n_3 ,


$$-i_3 - i_5 + i_6 = 0$$

$$-\frac{V_1 - V_3}{4} - \frac{V_2 - V_3}{8} + 2i_x = 0 \quad - \textcircled{3}$$

$$i_x = i_2 = \frac{V_1 - V_2}{2}$$

$$-\frac{V_1 - V_3}{4} - \frac{V_2 - V_3}{8} + V_1 - V_2 = 0 \quad - \textcircled{4}$$
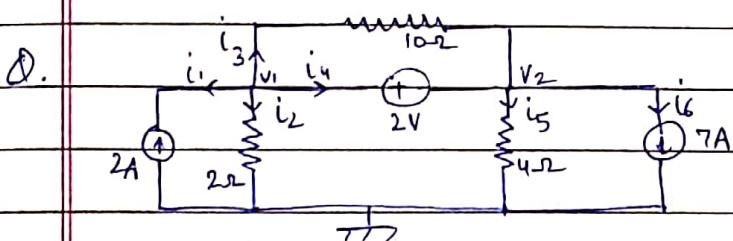
$$V_1 = 4.8 \text{ V} \quad V_2 = 2.4 \text{ V} \quad V_3 = -2.4 \text{ V}$$



Ans. At node n_1 ,

$$i_1 + i_2 + i_3 + i_4 = 0$$

$$-2 + \frac{V_1}{2} + \frac{V_1 - V_2}{10} + i_4 = 0 \quad - \textcircled{1}$$

At node n_2 ,

$$i_5 + i_6 - i_4 - i_3 = 0$$

$$\frac{V_2}{4} + 7 - i_4 - \frac{V_1 - V_2}{10} = 0 \quad - \textcircled{2}$$

$$\textcircled{1} + \textcircled{2}$$


~~$$-2 + \frac{V_1}{2} + \frac{V_1 - V_2}{10} + i_4 + \frac{V_2}{4} + 7 - i_4 - \frac{V_1 - V_2}{10} = 0$$~~

$$\frac{V_1}{2} + \frac{V_2}{4} = -5$$

$$2V_1 + V_2 = -20 \quad - \textcircled{3}$$

$$V_{\text{bus}} \text{ KVL}$$

$$+V_1 + V_2 - V_3 = 0$$

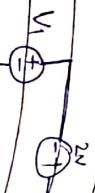


$$V_1 = -2.33V \quad V_2 = -5.33V$$

Supernode - When ever a voltage exist between non-reference nodes than that is known as super-node.

Mesh analysis

- Circuit variable current
- Applied only for planar N/w (Network)
- Variant of loop analysis
- Special case - Super mesh (current source - two mesh)
- Apply KVL around loop

Q. Find i_1 & i_2 ?

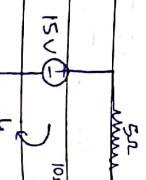

Ans.

$$\text{For loop 1} \quad 15 - 5i_1 - 10(i_1 - i_2) - 10 = 0 \quad \text{--- (1)}$$

For loop 2

$$10 - 10(i_2 - i_1) - 5i_2 - 5i_1 = 0 \quad \text{--- (2)}$$

$$i_1 = 1A$$

$$i_2 = 1A$$

DATE: / /

PAGE NO.:

Q. Find $i_1, i_2 \& i_3$?

Ans. For loop ①

$$24 - 10(i_1 - i_2) - 12(i_1 - i_3) = 0 - ①$$

For loop ②

$$-10(i_2 - i_1) - 24i_2 - 4(i_2 - i_3) = 0 - ②$$

For loop ③

$$-12(i_3 - i_1) - 4(i_3 - i_2) - 4I_o = 0 - ③$$

$$I_o = i_1 - i_2$$

$$i_1 = 2.25 \text{ A}$$

$$i_2 = 0.75 \text{ A}$$



$$i_3 = 1.5 \text{ A}$$

Q. Find currents?

Ans. For loop 1

$$-6i_1 + V_x - V_1 = 0 - ①$$

For loop 2

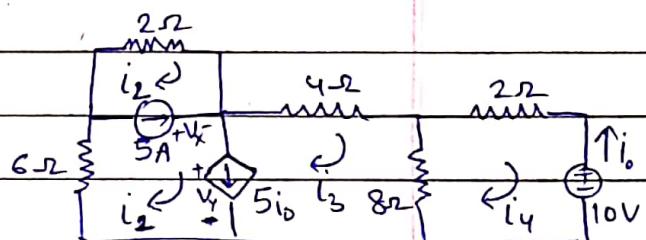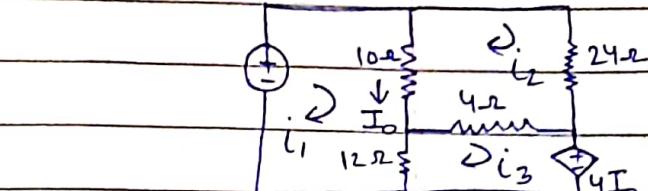

DATE : / /
PAGE NO. :

$$\Rightarrow -6i_1 - 2i_2 - 4i_3 - 8(i_3 - i_4) = 0$$

$$-6i_1 - 2i_2 - 12i_3 + 8i_4 = 0$$

$$i_1 = -7.5 \text{ A} \quad i_2 = -2.5 \text{ A} \quad i_3 = 3.93 \text{ A}$$

$$i_4 = 2.14 \text{ A}$$

Network Theorems

Superposition

Thevenin

Norton

Not for dependent sources. Any linear circuit can be transformed into the Thevenin equivalent circuit consisting of a current source in parallel with a resistance. This is in the form of a circuit (linear circuit) of a voltage source with a series resistance. with a current resp. steps -
1) The equivalent is the short circuit current due to each independent source. The open circuit voltage is the sum of voltages across all the elements of the circuit which we need to calculate.

2)


Repeat the above step with other independent sources.

3) Find the total contribution

by doing algebraic sum obtained by each independent sources.

d. Calculate V?

An. By superposition

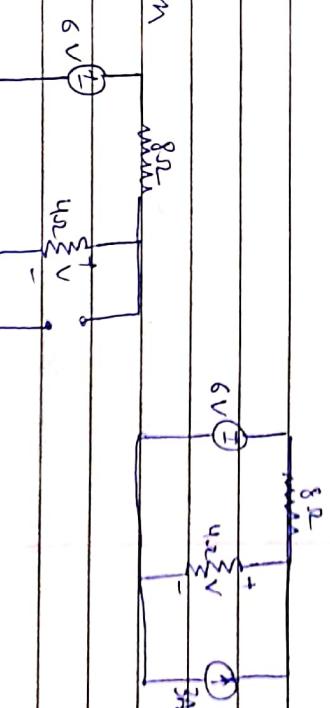

$$V_1 = \frac{6}{8+4} \times 4 = 2V$$

$$V_2 = \left(\frac{8}{8+4} \times 3 \right) \times 4 = 8V$$

$$V = V_1 + V_2$$

$$= 2 + 8 = 10V$$

By Thevenin

$$V_{oc} = 6 - (-24)$$

$$= 30V$$

$$R_{th} = 8\Omega$$

$$V = \frac{30}{8+4} \times 4 = 10V$$

4) Turn off all steps with other the independent sources.

By Norton
 $I_{SC} = 6 + 3$


$$= \frac{15}{4}$$

$$R_N = 8\Omega$$

$$I_2 = \frac{8}{8+4} \times \frac{15}{4}$$



$$= \frac{5}{2}$$

$$V = \frac{5}{2} \times 4 = 10V$$

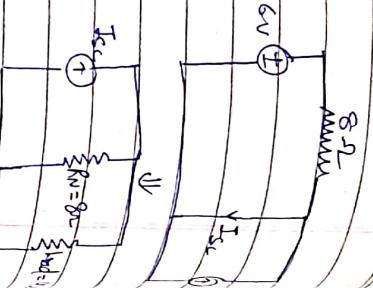

Q. Calculate i_o using superposition.

Ans.
By superposition

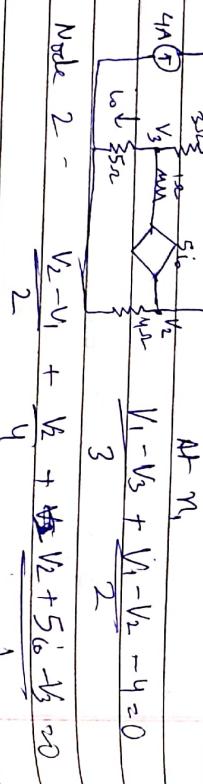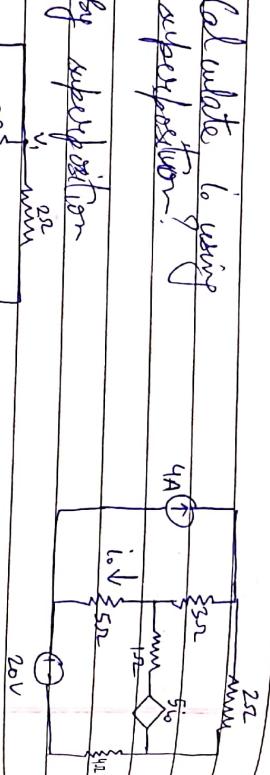

$$Node 2 - \frac{V_2 - V_1}{2} + \frac{V_2}{4} + \frac{V_2 + 5i_o - V_3}{1} = 0$$

$$Node 3 - \frac{V_3}{5} + \frac{V_3 + 5i_o - V_2}{1} + \frac{V_3 - V_1}{3} = 0$$

$$i_o = \frac{V_2}{5}$$

$$i_o = \frac{52}{17} A$$

Maximum Power Transfer Theorem

DATE : / /
PAGE NO. :

$$P = \frac{V_m^2}{R_L} \quad \text{--- (a)}$$

$$P = \left(\frac{V_m}{R_m + R_L} \right)^2 R_L \quad \text{--- (b)}$$

$$\frac{dP}{dR_L} = \left[(R_L + R_m)^2 \times 1 - R_L \cdot 2(R_m + R_L) \right] \frac{V_m^2}{(R_m + R_L)^4}$$

$$= \frac{R_m + R_L - 2R_L}{(R_m + R_L)^3} = \frac{R_m - R_L}{(R_m + R_L)^3} = 0$$

$$\Rightarrow R_L = R_m$$

$$P_{\text{max}} = V_m \times I_m$$

$$\text{Available power} = V_m \times \frac{V_m}{R_m + R_L}$$

$$= \frac{V_m^2}{R_m + R_L}$$

$$P_{\text{av}} = \frac{V_m^2}{R_m + R_L}$$

$$\Rightarrow \frac{V_m^2}{(R_m + R_L)^2} \times R_L = \frac{V_m^2}{4R_L} \times R_L$$

$$= \frac{V_m^2}{4R_L}$$


$$P_{\text{av}} = \frac{1}{2} P_{\text{max}}$$

Find V_{ab} ?


$$\text{Ans. } \frac{V-12}{6} + \frac{V}{12} + (-2) = 0$$

$$V = 16V$$

$$V_{ab} = 16 - (16) = 2.2V$$

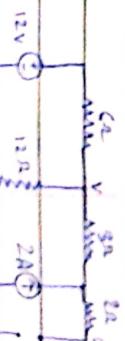

Reciprocity (V_A & I Interchangeable)

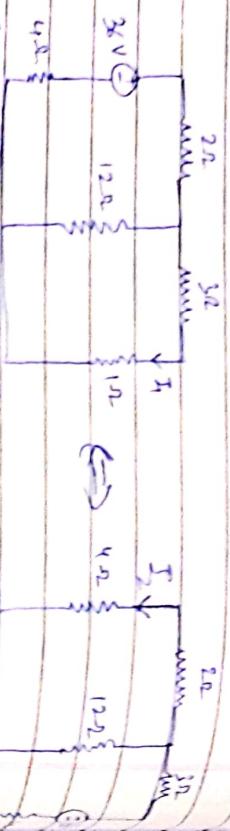

$$V - 3\Omega + V + 12\Omega = 0 \quad \text{Branch A}$$

$$\frac{V - 3}{12} + \frac{V + 12}{6} = 0 \quad \text{Branch B}$$

a.

$$V = 12V$$


$$I_1 = \frac{V - 0}{4} = \frac{12}{4} = 3A$$

$$I_2 = \frac{V + 12}{6} = \frac{12 + 12}{6} = 4A$$

Ans.

b.

$$V - 6 + \frac{V}{4} - 3 = 0$$

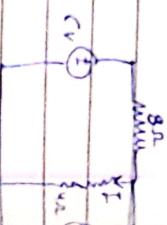

a.

$$V = 12V$$

$$I_1 = \frac{12 - 6}{4} = \frac{6}{4}V$$

Ans.

$$\frac{V - 6}{4} + \frac{V}{8} - 3 = 0$$


$$V = 10V$$

$$I_1 = \frac{V - 6}{4} = \frac{10 - 6}{4} = 1A$$

$$I_2 = \frac{V}{8} = \frac{10}{8}V$$

Source Transformation


DATE: / /
 PAGE NO.:

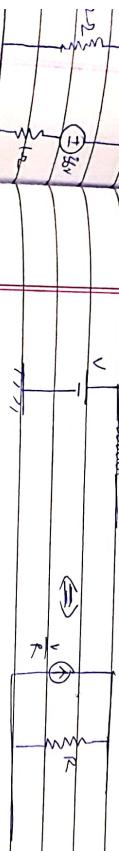

$$+L = 0$$

$$8V$$


$$3A$$

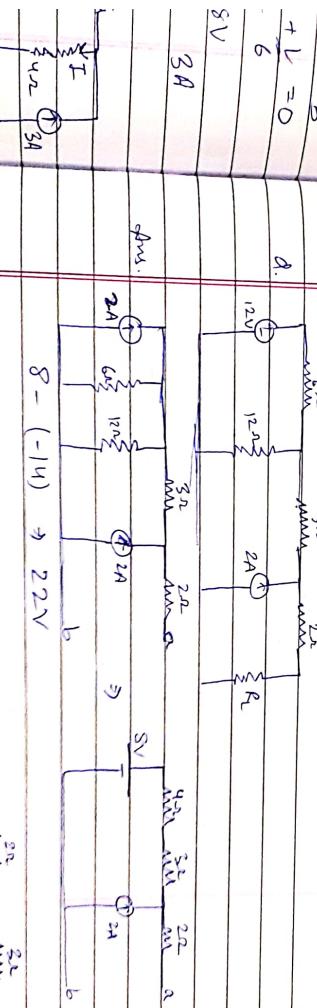

$$8 - (-14) \rightarrow 22V$$

a

Find V_o

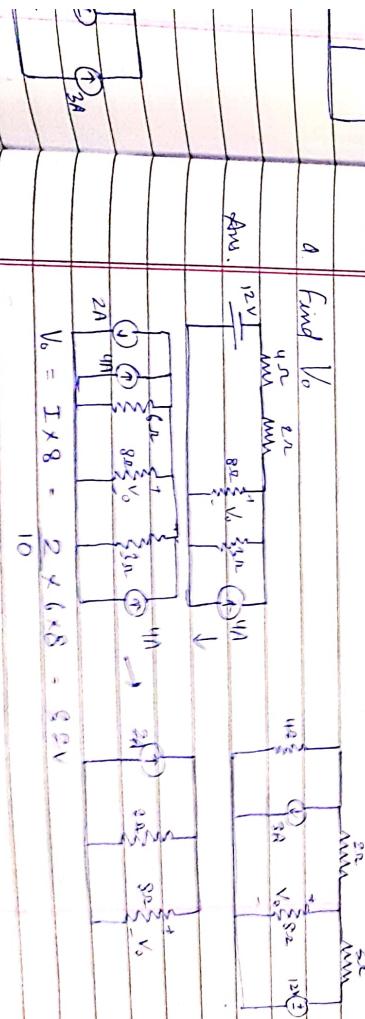

$$V_o = I \times 8 = 2 \times 6 \times 8 = 96V$$

10

Transients

D.C. Transients



\rightarrow Source free
 \rightarrow Forced Source

$\xrightarrow{\text{AC}} \xrightarrow{\text{DC}}$

$$R \rightarrow V = IR \rightarrow \text{Algebraic}$$

$$\left. \begin{array}{l} L \rightarrow V = L \frac{di}{dt} \\ C \rightarrow i = C \frac{dv}{dt} \end{array} \right\} 1^{\text{st}} \text{ order differential eq'}$$

Transient

$$t = 0^+ 0^-$$

$$\left. \begin{array}{ll} \text{Capacitor} & V_C \\ \text{Inductor} & I_0 \end{array} \right\}$$


Steady State

$$0^+ \infty$$

$$X_C = \frac{1}{2\pi f C} \quad t = 0 \rightarrow X_C = \infty$$

$$X_L = 2\pi f L \quad t = 0 \rightarrow X_L = 0$$

Source from R.C.

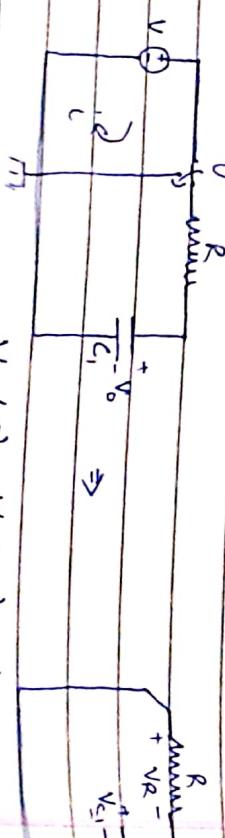

$$i_R + V_{C1} = 0 \Rightarrow C \frac{dV_{C1}}{dt} R + V_{C1} = 0$$

$$RC \frac{dV_{C1}}{dt} + V_{C1} = 0 \Rightarrow \frac{dV_{C1}}{dt} = -\frac{V_{C1}}{RC}$$

$$\int_0^{V(t)} \frac{dV_{C1}}{V_{C1}} = \int_0^t -\frac{1}{RC} dt$$

$$\Rightarrow \left[\ln V_{C1} \right]_0^{V(t)} = -\frac{1}{RC} [t]_0^t + \ln A$$

$$\ln V(t) = -\frac{1}{RC} t + \ln A$$

$$\frac{\ln V(t)}{A} = -\frac{t}{RC} \Rightarrow V(t) = A e^{-t/RC}$$

$$At t=0 \quad V(t) = V_0$$

$$V_0 = A e^{-t/RC} \Rightarrow A = V_0$$

$$V(t) = V_0 e^{-t/RC}$$

$$V(t) = V_0 e^{-t/\tau}, \quad \tau = RC \text{ (Time constant)}$$

$$i(t) = \frac{V(t)}{R} = \frac{V_0 e^{-t/RC}}{R}$$

$$P_R = i^2(t) R = \frac{V_0^2 e^{-2t/RC} \times R}{R^2}$$

$$P_R = \frac{V_0^2}{R} e^{-2t/RC}$$

$$W_R(t) = \int_0^t P_R dt$$

$$= \int_0^t \frac{V_0^2}{R} e^{-2t/RC} dt$$

$$= \frac{V_0^2}{R} \left[-\frac{1}{2} e^{-2t/RC} \right]_0^t = -\frac{V_0^2}{2R} R C \left[e^{-2t/RC} \right]^t_0$$

$$W_R(t) = -\frac{1}{2} C V_0^2 (e^{-2t/R_C} - 1)$$

$$W_R(t) = \frac{1}{2} C V_0^2 (1 - e^{-t/T})$$


$$V(t) = V_0 e^{-t/T}$$

$$V(0) = V_0$$

$$W_R(0) = \frac{1}{2} C V_0^2 = W_R(0)$$

$$W_R(\infty) = \frac{1}{2} C V_0^2 = W_R(0)$$

d. Find V_C, V_X, i_X for $t > 0$

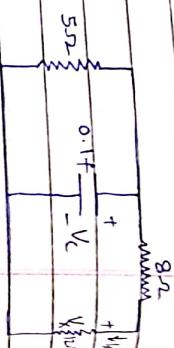

Ans.

$$V_C = V_0 e^{-t/R_C}$$

$$R_C + R = 5 \parallel (8+12) = 4 \Omega$$


$$R_C = 4 \times 0.1 = 0.4$$

$$V_C = 15 e^{-t/0.4}$$

$$V_X = \frac{12}{12+8} \cdot V_C = 9 e^{-2.5t} V$$

$$i_X = \frac{V_X}{12} = 0.7 e^{-2.5t} A$$

d. Find $V(t)$ for $t > 0$.

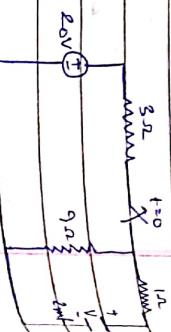

Ans.

$$V_0 = 15 V$$

$$V_t = 15 e^{-t/RC}$$

$$RC = 10 \times 2 \times 10^{-3} = 2 \times 10^{-2}$$

$$V(t) = 15 e^{-t/2 \times 10^{-2}}$$

$$W_R(0) = \frac{1}{2} C V_0^2 = 2.25 J$$


Source Free R.L. Circuit

$C \rightarrow$ Open Circuit

$L \rightarrow$ Short Circuit

$$i(0^-) = i(0^+) = I_0$$

$$\omega_0(L) = \frac{1}{2} L I_0^2$$

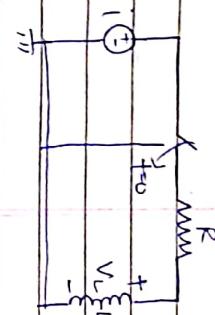

$$V_R + V_L = 0$$

$$iR + L \frac{di}{dt} = 0 \Rightarrow \frac{L di}{dt} = -iR$$

$$\frac{di}{dt} = -\frac{R}{L} i \Rightarrow \int_{I_0}^{i(t)} \frac{di}{i} = \int_0^t -\frac{R}{L} dt$$

$$\therefore \ln \frac{i(t)}{I_0} = -\frac{R}{L} t$$

$$i(t) = I_0 e^{-Rt/L}$$

$$i(t) = I_0 e^{-t/\tau} \text{ where } \tau = \frac{L}{R}$$

$$V(+)=i(t)R$$

$$= I_0 R e^{-t/\tau}$$

$$P = \frac{i^2 R}{I_0^2 R} e^{-2t/\tau}$$



$$WR(t) = \int_0^t P dt$$

$$= I_0^2 R \int_0^t e^{-2t'/\tau} dt'$$

$$= I_0^2 R \left(\frac{-1}{2} \times \frac{\tau}{2} \right) (e^{-2t/\tau})_0$$

$$WR(t) = \frac{1}{2} L I_0^2 (1 - e^{-2t/\tau})$$

$$W_R(\infty) = \frac{1}{2} L I_0^2 = W(0)$$

a) $I_o = 10A$ calculate $i(t)$, $i_x(t)$

$$i(t) = I_o e^{-iRT}$$

$$T = \frac{L}{R} = \frac{0.5}{R_m}$$

$$R_m = \frac{V_t}{i_t}$$



$$i + i_X + i_C = 0$$

$$i + \frac{V_t}{2} + V_t - \frac{3i}{4} = 0$$

$$-i_t + \frac{1}{2}V_t + \frac{1}{4}V_t + \frac{3}{4}i_t = 0$$

$$\left(\frac{1}{2} + \frac{1}{4}\right)V_t = \left(-\frac{3}{4} + 1\right)i_t$$

$$\frac{3}{4}V_t = \frac{1}{4}i_t$$

$$\frac{V_t}{i_t} = \frac{1}{3} = R_m$$

$$i(t) = 10e^{-t/1.5}$$

$$i_x(t)$$

$$= \frac{V_{22}}{2}$$


$$= \frac{L di/dt}{2} = 0.5 \times \frac{d}{dt}(10e^{-\frac{2}{3}t})$$

$$= \frac{0.5}{2} \times 10e^{-\frac{2}{3}t} \left(-\frac{2}{3}\right)$$

$$= -\frac{5}{3}e^{-\frac{2}{3}t}$$

$$= -\frac{5}{3}$$

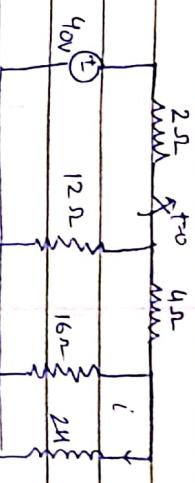Q. Switch open at $t = 0$. Calculate $i(t)$, $t > 0$



$$\text{Ans. } I_0 = 6A$$

$$i(t) = I_0 e^{-\frac{t}{T}}$$


$$T = \frac{L}{R} = \frac{2}{8} = \frac{1}{4}$$

$$R + R_m = 8\Omega$$

$$i(t) = 6 e^{-4t} V_A$$

$$= 6 e^{-4t} A$$

Q. Calculate V_x , $i(t)$, $I_0 = 7A$?

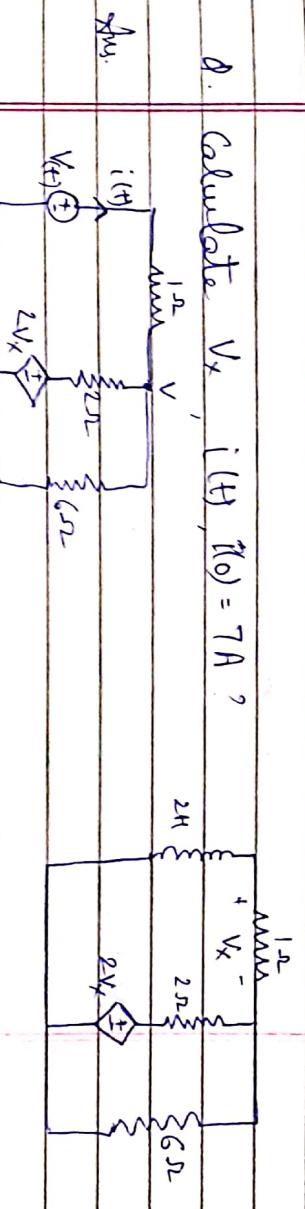

$$V - 2Vx + \frac{V - Vu}{2} + \frac{V}{6} = 0$$

$$V - Vu = -it \Rightarrow V = Vu - it$$

$$Vu = it$$

$$V - it - 2it + -it + \frac{Vu - it}{6} = 0$$

Q.

DATE : / /
PAGE NO. :

Forced Response


Singularity form \rightarrow Unit step signal $u(t)$
 \rightarrow Impulse $\delta(t)$
 \rightarrow Ramp $\gamma(t)$

Discontinuous in nature

Derivation (Derivative) is discontinuous

$$u(t) = \begin{cases} 0, & t < 0 \\ 1, & t \geq 0 \end{cases}$$
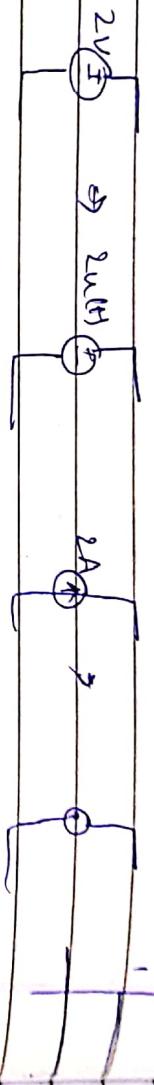
$$u(t) = \begin{cases} 0, & t < 0 \\ 1, & t \geq 0 \end{cases}$$



Natural Response

$$i(t) = I_0 e^{-t/\tau}, \quad \tau = \frac{L}{R} \Rightarrow L$$

$$V_L(t) = V_0 e^{-t/\tau}, \quad \tau = RC \Rightarrow C$$

Step response of RC circuit

$$V_S u(t) = \sqrt{R^2 + V_C^2}$$

$$= iR + V$$

$$\ln [V_{(+)}/V_S] - \ln [V_0/V_S] = -\frac{1}{RC}t$$

$$\ln \frac{V_t/V_S}{V_0/V_S} = -\frac{t}{RC}$$

$$\frac{V_t/V_S}{V_0/V_S} = e^{-t/RC}$$

$$V_t/V_S = (V_0/V_S) e^{-t/RC}$$

$$V_t = V_S + (V_0 - V_S) e^{-t/RC}$$

$$V_t = V_S + (V_0 - V_S) e^{-t/\tau}$$

↓

Total response Steady state response Transient response

$$V_t = V_{ao} + [V_0 - V_{ao}] e^{-t/RC}$$

$$V_t = V_0 e^{-t/RC} + V_S (1 - e^{-t/RC})$$

Total response → Natural response → forced Response
if $V_0 = 0$

A. At $t=0$ switch changes to B. Calculate $V(t)$ for $t = 1, 4 \text{ sec.}$

$$V_{in} = 15V$$

$$V(0) = V_{in} + [V(0) - V_{in}] e^{-\frac{t}{RC}}$$

$$V_{in} = 30V$$

$$T = RC$$


$$= \frac{1}{2} \times 10^3 \times 4 \times 10^3 = 2$$

$$V(1) = 30 - 15 e^{-\frac{1}{2}}$$

$$V(1) = 30 - 15 e^{-\frac{1}{2}} = 20.9V$$

$$V(4) = 30 - 15 e^{-2} = 27.9V$$

D. Calculate $i_A V$ for $t > 0$

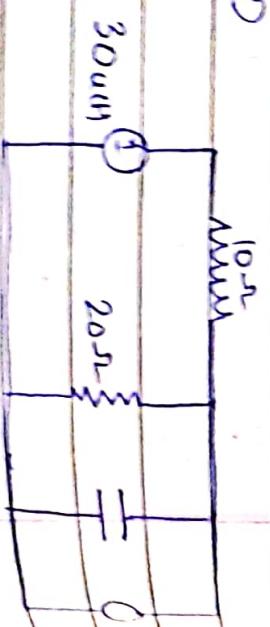

Step Response of RLC

$$\text{Let } I_L(0^-) = I_L(0^+), \quad I_o$$

$$V(t) = V_{(0)} + [V_{(0)} - V_{(0)}] e^{-t/\tau}$$

$$= V_0 e^{-t/\tau} + V_s (1 - e^{-t/\tau})$$

$$I_{s u(t)} = i(R + L)$$

$$= \frac{V_i}{R} + i$$

$$= \frac{L}{R} \frac{di}{dt} + i$$

$$\frac{L}{R} \frac{di}{dt} = I_{s u(t)} - i$$

$$\frac{di}{dt} = \frac{R}{L} dt$$

$$I_{s u(t)} - i$$

$$\frac{di}{i - I_{s u(t)}} = -\frac{R}{L} dt$$

$$\int_{I_o}^{i(t)} \frac{di}{i - I_{s u(t)}} = -\frac{R}{L} \int_0^t dt$$

$$\int_{I_o}^{i(t)} \frac{di}{i - I_o} = -\frac{R}{L} \int_0^t dt$$

$$[R_n(i - I_o)]_{I_o}^{i(t)} = -\frac{R}{L} [t]_0^t$$

$$R_n i(t) - R_n I_o = -\frac{R}{L} t$$

$$i(t) - I_o = e^{-R_n t}$$

$$I_o - I_s$$

$$i(t) = I_s + (I_o - I_s) e^{-R_n t}$$

$$= \frac{V_s}{R} + (I_o - \frac{V_s}{R}) e^{-R_n t}$$

Q.2 Find $i(t)$ at $t=0$, $I(\infty)$,

R_{in} , T , $i(t)$?

$\Delta - 3.$ Circuit S_1 closed at $t=0$
 S_2 closed at $t=4$ sec
 Find $i(0)$, $i(2)$, $i(5)$

Ans - 3. ~~$i(t) = 0$~~ $0 \leq t \leq 4$

$i_0 = 0$
 Only S_1 is closed

$$i(t) = i(4) + (i_0 - i(4)) e^{-\frac{t}{T}}$$

$$= 4 + (0 - 4) e^{-\frac{t}{2}}$$

$$= 4(1 - e^{-\frac{t}{2}})$$

$$4 \leq t < \infty$$

$$\cancel{i(t)} = i(t) = 2.92 + 1.27 e^{-1.46} \text{ (Ans)}$$

$$i(2) = 4(1 - e^{-1})$$


Initial and final values (Transient and steady state)


$$+ = 0^- / 0^+$$

$$R \rightarrow \frac{dV_R}{dt} \rightarrow V_R \rightarrow KVL, KCL \rightarrow \frac{dV_R}{dt}, \frac{dV_R}{dt}|_{t=0}$$

$$L \rightarrow i(0^-) = i(0^+) = I_0 \text{ (natural)}$$

$$V_L = L \frac{di}{dt} \quad \frac{di}{dt}|_{t=0^+} \rightarrow \text{loop} \rightarrow V_L = \frac{di}{dt} = \frac{V_L}{L}$$

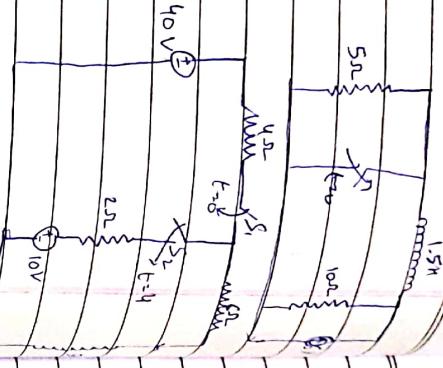

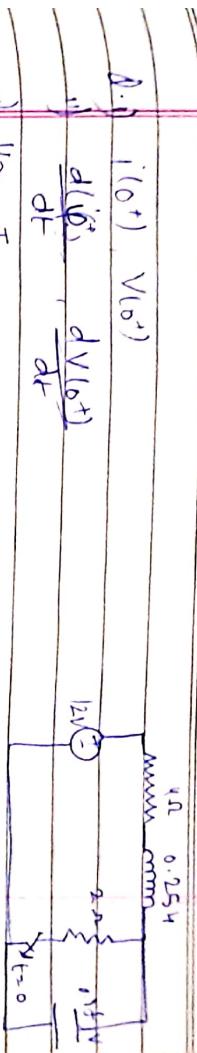

$$\text{Ans. 1} \quad t < 0$$

$$i(0^+) = \frac{R}{L} = \frac{2\Omega}{0.25H} = 8A$$

$$v(0^+) = 2 \times 8 = 16V$$

$$V_L = L \frac{di}{dt}$$

$$\frac{di}{dt} = \frac{V_L}{L}$$

$$12 = V_L + V_C$$

$$12 = V_{L0^+} + V_{C0^+}$$

$$12 = i(0^+) \times 4 + V_{C0^+}$$

$$12 = 4 \times 8 + V_{C0^+}$$

$$12 = 32 + V_{C0^+}$$

$$V_{C0^+} = 12 - 32 = -16V$$

$$\frac{di(0^+)}{dt} = \frac{V_L}{L} = \frac{16}{0.25} = 64A$$

$$i = \frac{CdV}{dt} = \frac{dV}{dt} \cdot \frac{1}{C}$$

$$= \frac{2}{0.1}$$

$$= 20V/Sec.$$


$$i(0) = 0 \quad v(0) = 12V$$

d. Calculate

i(0⁺), V_L(0⁺), V_R(0⁺)

$\frac{di}{dt}(0^+)$, $\frac{dV_L}{dt}(0^+)$, $\frac{dV_R}{dt}(0^+)$

i(∞), V_L(∞), V_R(∞)

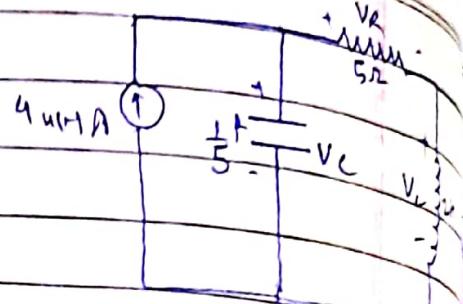

Aus. i) i(0⁺) = -6 A

V_L(0⁺) = 0 A

V_R(0⁺) = 0

ii) $V_L = 1 \frac{di}{dt}$, $\frac{di}{dt} = \frac{4 \times 10^{-3}}{R} = \frac{V_L}{R} = \frac{0}{R} = 0$

V_C = V_R + V_L

V_C = V_C - V_R

= 0 - (5 × 25 × 2)

Source free RLC

Let i(0⁻) = i(0⁺) = I₀

V(0⁻) = V(0⁺) = V₀

Using KVL


$$V_R + V_L + V_C = 0$$

$$iR + L \frac{di}{dt} + \frac{1}{C} \int i dt = 0$$

$$R \frac{di}{dt} + L \frac{d^2i}{dt^2} + \frac{i}{C} = 0$$

$$\frac{d^2i}{dt^2} + \frac{R}{L} \frac{di}{dt} + \frac{1}{LC} = 0$$

$$i = A e^{st}$$

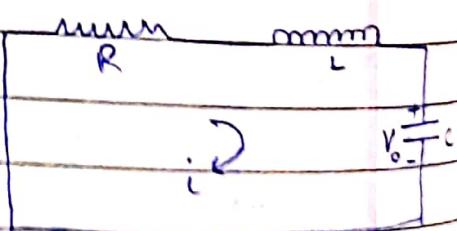

$$\frac{d^2}{dt^2} (Ae^{st}) + \frac{R}{L} \frac{d}{dt} (Ae^{st}) + \frac{Ae^{st}}{LC} = 0$$

$$As^2 e^{st} + \frac{R}{L} s A e^{st} + \frac{Ae^{st}}{LC} = 0$$

$$Ae^{st} \left(s^2 + \frac{R}{L}s + \frac{1}{LC} \right) = 0$$

$$i = Ae^{st} \neq 0$$

$$s^2 + \frac{Rs}{L} + \frac{1}{LC} = 0$$

$$b = \frac{R}{L}, c = \frac{1}{LC}, a = 1$$

$$S_{1,2} = \frac{-b \pm \sqrt{b^2 - 4ac}}{2a}$$

$$= \frac{-R}{2L} \pm \sqrt{\left(\frac{R}{L}\right)^2 - \frac{4}{LC}} = \frac{-R}{2L} \pm \sqrt{\left(\frac{R}{2L}\right)^2 - \frac{1}{LC}}$$

$$S_{1,2} = \frac{-R}{2L} \pm \sqrt{\left(\frac{R}{2L}\right)^2 - \frac{1}{LC}}$$

$$\text{Assume } \alpha = \frac{R}{2L} \quad \text{so } \omega_0 = \frac{1}{\sqrt{LC}}$$

$\alpha \rightarrow$ damping factor

ω_0 = undamped natural frequency / resonant freq.

$$\alpha > \omega_0$$

$S_{1,2}$ = discrete
distinct real

$$i(t) = A_1 e^{s_1 t} + A_2 e^{s_2 t}$$

Overdamped

$$\alpha = \omega_0$$

$S_{1,2}$ = real and
equal

$$i(t) = (A_1 + A_2 t) e^{-\alpha t}$$




Critically damped

$$\alpha < \omega_0$$

complex & comp. pair
 $i = e^{-\alpha t} (\cos \omega t + \sin \omega t)$

$$\omega_d = \sqrt{\omega_0^2 - \alpha^2}$$

Under damped

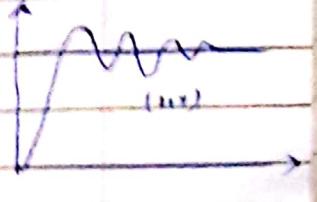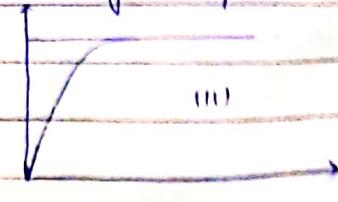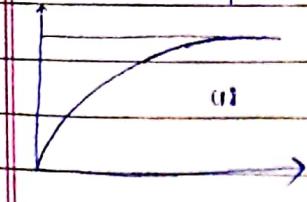

2. Calculate α & ω_0

3. Compare α & ω_0 to write $i(t)$

4. Calculate $S_{1,2} \rightarrow$ roots of characteristic equation

5. calculate constant A_1, A_2 using initial condition
a derivative

Q. Cal. $\frac{di}{dt}$

$\frac{di}{dt}$

Ans.

$$V_R + V_L = V_u + V_C$$

$$V_C(0^+) + \frac{1}{C} \frac{di}{dt} = V_u(0^+) + V_C(0^+)$$

$$6 \times 2 + 2 \times \frac{di}{dt} = 4 \times (-2) + 12$$

$\frac{di}{dt}$

$$\frac{di(0^+)}{dt} = -4 \text{ P/sec.}$$

Source free RLC circuit

i) Series RLC

$$\alpha = \frac{R}{2L} \quad \omega_0 = \sqrt{\frac{1}{LC}}$$

$$\begin{aligned} \text{Wd} &= \sqrt{\omega_0^2 - \alpha^2} \\ i(t) &= A_1 e^{s_1 t} + A_2 e^{s_2 t} \rightarrow \text{overdamped} \\ &= (A_1 + A_2) e^{-\alpha t} \rightarrow \text{critically damped} \\ &= e^{-\alpha t} (A_1 \cos \omega_d t + A_2 \sin \omega_d t) \rightarrow \text{Underdamped} \end{aligned}$$

2) Parallel RLC

$$i_R + i_L + i_C = 0$$



$$\frac{V_R}{R} + \frac{1}{L} \int V dt + \frac{C dV}{dt} = 0$$

$$\frac{V}{R} + \frac{1}{L} \int V dt + \frac{C dV}{dt} = 0$$

$$\frac{1}{R} \frac{dV}{dt} + \frac{1}{L} V + \frac{C d^2 V}{dt^2} = 0$$

$$\frac{d^2 V}{dt^2} + \frac{1}{L} \frac{dV}{dt} + \frac{V}{RC} = 0$$

$$V = A e^{s t}$$

$$\frac{d^2 (A e^{s t})}{dt^2} + \frac{1}{RC} \frac{d (A e^{s t})}{dt} + \frac{A e^{s t}}{LC} = 0$$

$$A s^2 e^{s t} + \frac{1}{RC} A s e^{s t} + \frac{A e^{s t}}{LC} = 0$$

$$A e^{s t} \left(s^2 + \frac{1}{RC} + \frac{1}{LC} \right) = 0$$

$$\text{Since } A e^{s t} \neq 0$$

$$s^2 + \frac{1}{RC} + \frac{1}{LC} = 0$$

$$lefF \alpha = \frac{1}{2RC} \quad , \quad \omega_0 = \frac{1}{\sqrt{LC}}$$

$$= \frac{1}{2T}$$

$$\omega_{1,2} = -\alpha \pm \sqrt{\alpha^2 - \omega_0^2}$$


$$\alpha > \omega_0$$

$$\alpha = \omega_0$$

distinct

$$V(t) = A_1 e^{S_1 t} + A_2 e^{S_2 t}$$

$$V(t) = (A_1 + A_2) e^{-\alpha t}$$

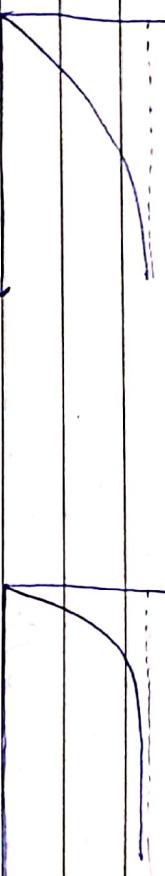

Overdamped

Critically damped

$$\alpha < \omega_0$$

Complex Conjugate

$$V(t) = e^{-\alpha t} (A_1 \cos \omega t + A_2 \sin \omega t)$$

$$\omega_d = \sqrt{\omega_0^2 - \alpha^2}$$

Underdamped

Steps -

$$1) \quad t < 0 \quad - \text{Cal. } I_0, V_0$$

$$2) \quad t = 0 \quad - \frac{dI}{dt}, \frac{dV}{dt}$$


$$3) \quad t > 0 \quad - ① \text{ cal. } \alpha, \omega_0$$

$$② \quad V(t)$$

$$③ \quad A_1, A_2$$

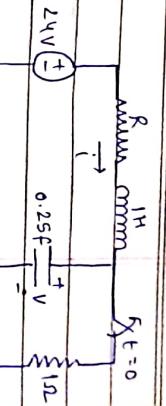a. For $t > 0$, calculate $i(t)$

$$R = 5\Omega, R = 4\Omega, L = 1\Omega$$



$$i(0^-) = i(0^+) = I_0 = 4A$$

$$V(0^-) = V(0^+) = V_0 = 4V$$

$$\frac{di}{dt} (t=0) \rightarrow 24 \neq 4R + V_L + V_C \quad \text{not equal}$$


$$t > 0, \alpha = \frac{R}{2L} = 2.5 \quad \left. \begin{array}{l} \alpha > \omega_0 \\ \text{Overdamped} \end{array} \right\}$$

$$\omega = \frac{1}{\sqrt{LC}} = 2 \quad \left. \begin{array}{l} \alpha > \omega_0 \\ \text{Overdamped} \end{array} \right\}$$

$$R = 4\Omega \rightarrow Critically \quad \alpha = \omega_0$$

$$R = 1\Omega \rightarrow \alpha < \omega_0 \quad \text{Underdamped}$$

b. Cal. $V(t)$ for $t > 0$

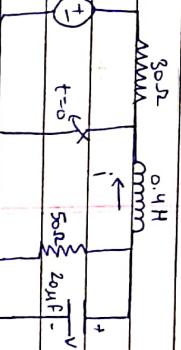

$$i(0^-) = -0.5A$$

$$V(0^-) = 25V$$

$$i + i_R + i_C = 0$$

$$-0.5 + \frac{V_L}{50} + \frac{dV_C}{dt} = 0 \rightarrow \frac{dV}{dt} = 0$$

$$t > 0,$$

$$\alpha = \frac{1}{2RC} = \frac{1}{2 \times 50 \times 2 \times 10^{-6}} = 500$$

$$\omega = 3.54$$

$$\alpha > \omega_0 \rightarrow \text{Overdamped}$$

$$S_{1,2} = -\alpha \pm \sqrt{\alpha^2 - \omega_0^2}$$

$$+ \frac{R}{V_{in}} \rightarrow V_{out} = \frac{j\omega C}{R + j\omega C} V_{in}$$

$$\text{Ans} - \frac{V_o}{V_{in}} = \frac{1}{1 + j\omega RC} = \frac{1}{1 + j\omega C} S = j\omega$$

$$H(\text{gain}) = \left| \frac{V_o}{V_{in}} \right| = \frac{1}{1 + \omega^2 RC} S = j\omega$$

$$\phi = -\tan^{-1}(\omega RC)$$

$$+ \frac{1}{V_{in}} R_{in} + V_{out} = \frac{R}{R + j\omega C} V_{in} = \frac{1}{1 + j\omega RC} V_{in}$$

$$V_{out} = \frac{1}{1 + \frac{1}{SRC}} V_{in}$$

$$V_o = \frac{1}{1 - j\omega RC} \Rightarrow \left| \frac{V_o}{V_{in}} \right| = \frac{1}{1 + \left(\frac{1}{\omega RC} \right)^2}$$

$$\phi = -\tan^{-1} \left(\frac{-1}{\omega RC} \right)$$

$$= \tan^{-1} \left(\frac{1}{\omega RC} \right) \uparrow \text{Ans}$$

Half Bridge Transistor



$$P_{out} = \frac{P_{in}}{2} \quad dB = 10 \log_{10} \left(\frac{P_o}{P_{in}} \right)$$

$$V_{out}^2 = \frac{V_{in}^2}{2} = 10 \log_{10} \left(\frac{V_o}{V_{in}} \right)^2$$

$$V_{out} = \frac{V_{in}}{\sqrt{2}} = 20 \log_{10} \left(\frac{V_o}{V_{in}} \right)$$

$$\frac{V_{out}}{V_{in}} = \frac{1}{\sqrt{2}} \quad LT = \frac{(s+3)}{(s+4)} = \frac{(3+j\omega)}{(4+j\omega)} \rightarrow +20dB/sec$$

Step Response of Series RLC

$$\begin{aligned} KVL \rightarrow & V_R + V_L + V_C = V_S \\ iR + L \frac{di}{dt} + \frac{1}{C} \int v \, dt &= V_S \end{aligned}$$

$$RC \frac{dv}{dt} + LC \frac{d^2v}{dt^2} + v = V_S$$

$$\frac{d^2v}{dt^2} + \frac{R}{L} \frac{dv}{dt} + \frac{1}{LC} v = \frac{V_S}{LC}$$

Non Homogeneous $\rightarrow RHS \neq 0$

$$\text{Total Solution} = C.F. + P.I.$$

$$LHS \quad RHS$$

$$\text{Equality RHS} = 0 \quad \frac{RHS}{C.F.}$$

$$\frac{d^2V}{dt^2} + \frac{R}{L} \frac{dV}{dt} + \frac{V}{LC} = \frac{V_0}{LC}$$

$$C.F. \Rightarrow \frac{d^2V}{dt^2} + \frac{R}{L} \frac{dV}{dt} + \frac{V}{LC} = 0 \rightarrow / \frac{R^2 + RL}{L}$$

$$i(t) = A_1 e^{S_1 t} + A_2 e^{S_2 t}$$

$$V(t) = A_1 e^{S_1 t} + A_2 e^{S_2 t}$$

$$P.I. = \frac{V_s}{LC} = \frac{V_s}{(1 + RCD + LCD^2)}$$

$$= \frac{V_s}{LC} (1 + RCD + LCD^2)^{-1}$$

$$= V_s (1 - RCD + LCD^2 - \dots)$$

$$= V_s - 0 - 0$$

$$= V_s$$

$$V(t) = A_1 e^{S_1 t} + A_2 e^{S_2 t} + V_s \quad \text{Overdamped (critically)} \quad \omega < \omega_0 \quad \omega = \omega_0$$

$$= V_t(t) + V_s(t)$$

Transient

Steady State

$$i_R + i_L + i_C = I_s$$

$$\frac{V}{R} + i_L + C \frac{dV}{dt} = I_s$$

$$\frac{L}{R} \frac{di}{dt} + i + C \frac{d}{dt} \left(\frac{L}{R} \frac{di}{dt} \right) = I_s$$

$$LC \frac{d^2i}{dt^2} + \frac{L}{R} \frac{di}{dt} + i = I_s$$

$$\frac{d^2i}{dt^2} + \frac{1}{RC} \frac{di}{dt} + \frac{i}{LC} = \frac{I_s}{LC}$$

General sol. = C.F. + P.I.

$$i(t) = A_1 e^{S_1 t} + A_2 e^{S_2 t} + I_s$$

Series RLC

$$\alpha = \frac{R}{2L} \quad \omega_0 = \frac{1}{\sqrt{LC}} \quad \omega_d = \sqrt{\omega_0^2 - \alpha^2}$$

Source free

$$i(t) = A_1 e^{S_1 t} + A_2 e^{S_2 t}$$

$$\alpha > \omega_0$$

$$\alpha = \omega_0$$

$$\alpha < \omega_0$$


$$i(t) = A_1 e^{S_1 t} + A_2 e^{S_2 t}$$

$$i(t) = (A_1 + A_2 t) e^{-\alpha t}$$

$$i(t) = e^{-\alpha t}$$

$$(A_1 \cos \omega_0 t + A_2 \sin \omega_0 t)$$

d. Calculate $V(t)$, $I(t)$ for $t > 0$

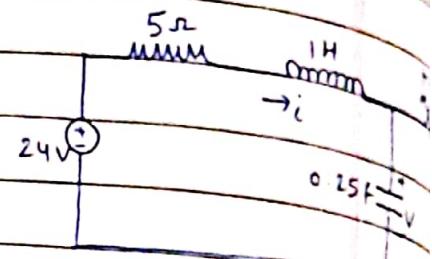

$$\text{Ans. } I_0 = 4A$$

$$V_0 = 4V$$

$$V(t) = A_1 e^{S_1 t} + A_2 e^{S_2 t} + 24$$

$$\alpha = 2.5, \omega_0 = 2 \quad 3\alpha > \omega_0$$

$$S_{1,2} = -\alpha \pm \sqrt{\alpha^2 + \omega_0^2}$$

$$= -1, -4$$

$$\frac{dV}{dt}(t=0) = 16$$

$$i(0) = C \frac{dv}{dt}$$

$$V(t) = A_1 + A_2 + 24 = 4$$

$$A_1 + A_2 = -20 \quad \textcircled{1}$$

$$\frac{dV(t)}{dt} = -A_1 e^{-t} - 4A_2 e^{-4t}$$

$$16 = -A_1 - 4A_2 \quad \textcircled{2}$$

$$A_1 = -\frac{64}{3}, \quad A_2 = \frac{4}{3}$$


$$V(t) = -\frac{64}{3}e^{-t} + \frac{4}{3}e^{-4t} + 24$$

$$i(t) = C \frac{dV(t)}{dt}$$

$$= \frac{1}{4} \left(\frac{64}{3}e^{-t} - \frac{16}{3}e^{-4t} + 0 \right)$$

$$= \frac{16}{3}e^{-t} - \frac{4}{3}e^{-4t} \text{ A}$$

d. Calculate $V(t)$, $I(t)$ for $t > 0$

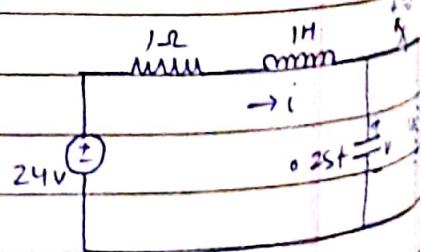

$$\text{Ans. } I_0 = 12A$$

$$V_0 = 12V$$


$$V(t) = e^{-\alpha t} (A_1 \cos \omega_0 t + A_2 \sin \omega_0 t) + 24$$

$$= e^{-0.5t} (A_1 \cos(1.93)t + A_2 \sin(1.93)t)$$

$$\alpha = 0.5 \quad \left. \right\} \alpha < \omega_0$$

$$\omega_0 = \frac{2}{2}$$

Q. Find expression in 2nd derivative.

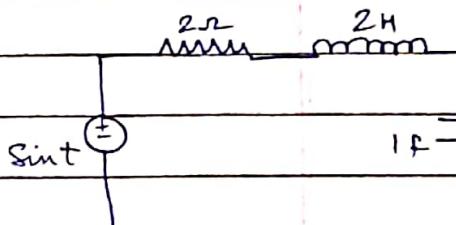


$$\text{Ans. } V_R + V_L + V_C = \text{Sint}$$

$$iR + L \frac{di}{dt} + \frac{1}{C} \int i dt = \text{Sint}$$

$$\frac{L di}{dt} + L \frac{d^2 i}{dt^2} + \frac{i}{C} = \text{Cost}$$

$$\rightarrow \frac{2 di}{dt^2} + 2 \frac{di}{dt} + i = \text{Cost}$$

Q. Calculate $i(0), V(0)$.

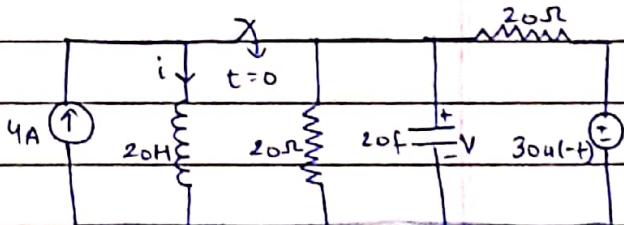


$$\text{Ans. } u(t) = \begin{cases} 0, & t < 0 \\ 1, & t \geq 0 \end{cases}$$


$$u(t) = \begin{cases} 0, & t > 0 \\ 1, & t \leq 0 \end{cases}$$

$$t < 0, \quad i(0) = 4A$$

$$V(0) = 15V$$

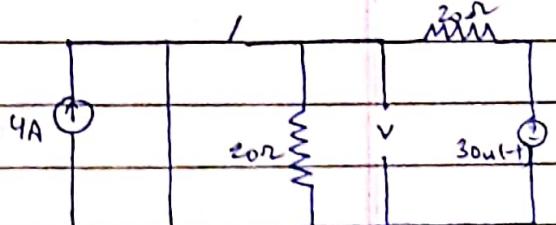

$$t = 0, \quad V = L \frac{di}{dt}$$

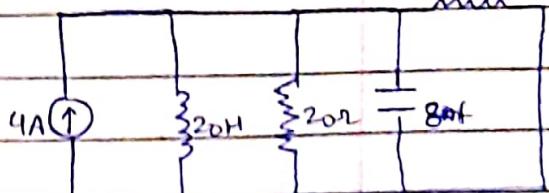

$$\frac{di}{dt}(t=0) = \frac{V_L(0)}{L} = \frac{15}{20} = \frac{3}{4}$$

$$\alpha = \frac{1}{2RC} = \frac{1}{2 \times 10 \times 8 \times 10^{-3}} = 6.25$$

$$\omega = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{20 \times 8 \times 10^{-3}}} = 2.5$$

$\alpha > \omega \rightarrow \text{overdamped}$

$$S_{1,2} = -\alpha \pm \sqrt{\alpha^2 - \omega_0^2}$$

$$= -11.928, -0.5218$$

$$i(t) = A_1 e^{-11.928t} + A_2 e^{-0.5218t} + 4$$

$$i(0) = A_1 + A_2 + 4$$

$$4 = A_1 + A_2 + 4$$

$$A_1 + A_2 = 0 \quad \text{--- (1)}$$


$$\frac{di(t)}{dt} = -11.928 A_1 e^{-11.928t} + (-0.5218) A_2 e^{-0.5218t}$$

$$\frac{3}{4} = -11.928 A_1 - 0.5218 A_2 \quad \text{--- (2)}$$

$$A_1 = 0.2055 \quad A_2 = -0.0655$$

Q. Calculate $i(t)$ & $V(t)$ for $t > 0$

Ans. $\alpha = \frac{1}{2PC} = 0$

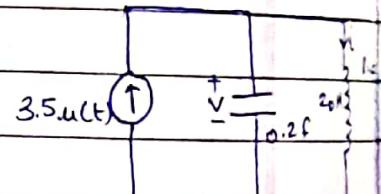


$$\omega = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{20 \times 0.2}} = \frac{1}{2}$$

$\omega > \alpha \rightarrow \text{underdamped}$

$$i(t) = 3.5(1 - \cos 0.5t) A$$

$$V(t) = 1.75 \sin 0.5t$$

Q. Find $i(t)$ & $V(t)$ for $t > 0$

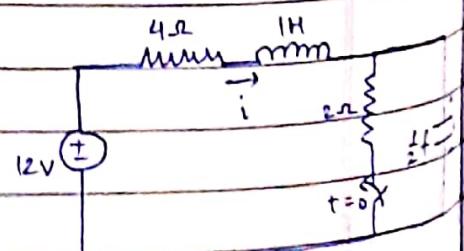

Ans. $i(0) = 0$

$$V(0) = 12$$

Step 1 - Calculate initial conditions.

Step 2 - Calculate $x(t)$ by turning off independent source. i.e. $\frac{d^2v}{dt^2} \leftarrow KCL$ and $\frac{d^2i}{dt^2} \leftarrow KVL$

Step 3 - Calculate $x(\infty)$

Step 4 - Total response = $x_t(t) + x(\infty)$

Step 5 - Constants using initial conditions


$$(a) i_L(t=0) = \frac{v_L}{L} = \frac{12 - 4i(0) - V}{L} = \frac{12 - 0 - 12}{L} = 0$$

$$\frac{dv(t=0)}{dt} = \frac{i_c}{C} = \frac{-6}{1/2} = -12 \text{ V/sec.}$$

$$-i + \frac{v}{2} + i_c = 0 \Rightarrow i_c = i - \frac{v}{2} = 0 - \frac{12}{2} = -6$$

$$(3) KCL \rightarrow -i + \frac{v}{2} + i_c = 0$$

$$i = \frac{v}{2} + C \frac{dv}{dt}$$

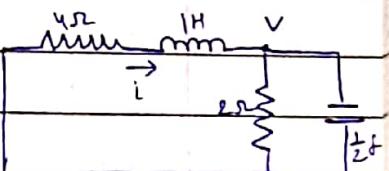

$$KVL \rightarrow -4i - v_L - v_C = 0$$

$$-4i - L \frac{di}{dt} - V = 0$$

$$-4\left(\frac{v}{2} + \frac{1}{2} \frac{dv}{dt}\right) - L \frac{d}{dt} \left(\frac{v}{2} + \frac{1}{2} \frac{dv}{dt}\right) - V = 0$$

$$\Rightarrow -2V - 2 \frac{dv}{dt} - \frac{1}{2} \frac{dv}{dt} - \frac{1}{2} \frac{d^2v}{dt^2} - V = 0$$

$$\Rightarrow \frac{d^2v}{dt^2} + 5 \frac{dv}{dt} + 6V = 0 \rightarrow V_t$$

$$S_{1,2} = -2, -3$$

$$V_{ss}(\infty) = 4V$$

$$V(t) = V_t(t) + V_{ss}(t)$$

$$= A_1 e^{-2t} + A_2 e^{-3t} + U$$

Sinusoidal and Phasors


$$f(t) = \sin t$$

$$T_w = 2\pi$$

$$f(t+T) = \sin \omega(t+T)$$

$$= \sin(\omega t + \omega T)$$

$$= \sin \omega t$$

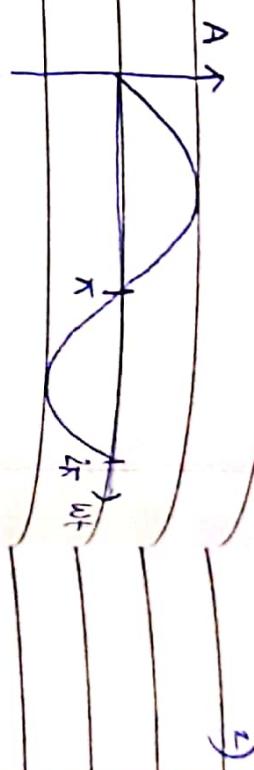

Cycle \rightarrow 1 wave
 $T \rightarrow$ Time period
 $f \rightarrow$ cycle/sec

Phase is the anti clockwise rotating vector in and the

1) Across R

$$i = \text{In coswt}$$

$$i = \text{In coswt}$$

$$V = \text{In R coswt}$$

$$V_L = \text{In R coswt}$$

$$V_L = \text{In R coswt}$$

2) Across L

$$i = \text{Im cos}(\omega t + \phi)$$

$$i = \text{Im cos}(\omega t + \phi)$$

$$V = L \text{Im}(-\omega \sin(\omega t + \phi))$$

$$V = -\omega L \text{Im} \sin(\omega t + \phi)$$


$$= -\omega L \text{Im} \sin(\omega t + \phi - \pi)$$

$$= -\omega L \text{Im} \sin(\phi - \pi)$$

$$= -\omega L \text{Im} \cos(\omega t + \phi - \pi)$$

$$= -\omega L \text{Im} \cos(\omega t + \phi)$$
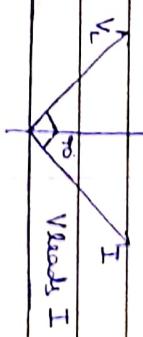
$$V = (j\omega L) \text{Im} \cos(\omega t + \phi)$$



Phasor

Representation \rightarrow rectangular $\rightarrow \alpha + j\beta$

$$\rightarrow \text{polar} \rightarrow r \angle \phi \quad \text{where} \quad r = \sqrt{\alpha^2 + \beta^2}$$

$$\phi = \tan^{-1}(\frac{\beta}{\alpha})$$

\rightarrow Exponent form $\rightarrow r e^{j\phi}$, $e^{j\phi} = \cos\phi + j \sin\phi$

$$j^2 = -1 \quad j = \sqrt{-1}$$

3)

Across C

$$i = C \frac{dV}{dt}$$

$$\frac{1}{C}$$

$$= \omega C V_m \angle 90^\circ$$

Current leads Voltage



Impedance (Z)

1) Resistor

$$i = I_m \cos \omega t$$

$$Z = \frac{V}{I} = R \Omega$$

2) Inductor

$$i = I_m \cos \omega t$$

$$= I_m L_o$$

$$Z = \frac{V}{I} = j\omega L \Omega$$

$$= \omega L I_m e^{j\omega t}$$

$$= \omega L (0 + j + 1)$$

$$Z = \frac{V}{I} = j\omega L \Omega$$

3) Capacitor

$$V = V_m \cos \omega t$$

$$i = \omega C V_m e^{j\omega t}$$

$$= \omega C V_m (0 + j)$$

$$Z = \frac{V}{I} = \frac{1}{j\omega C}$$

$$Z = -\frac{1}{\omega C} \Omega$$

→ for addition, subtraction use rectangular form
for multiplication, division use polar form

$$V = V_{m_1} \cos(\omega t + \phi_1) + V_{m_2} \cos(\omega t + \phi_2) + \dots - V_{m_n} \cos(\omega t + \phi_n)$$

$$= V_{m_1} e^{j(\omega t + \phi_1)} + V_{m_2} e^{j(\omega t + \phi_2)} + \dots + V_{m_n} e^{j(\omega t + \phi_n)}$$


D. Calculate $i(t)$, $v(t)$

Ans.


$$i = \frac{v}{2} = \frac{4 \cos 5t}{2 + j5} = \frac{4 \angle 0^\circ}{\sqrt{29} \cdot \tan\left(\frac{\pi}{2}\right)} = \frac{4}{5.4} \angle -\tan\left(\frac{\pi}{2}\right)$$

$$\omega = 50 \text{ rad/sec.}$$

Calculate Total Impedance

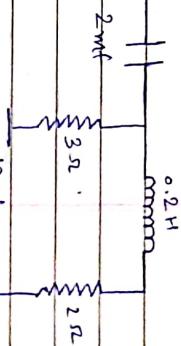

① Mesh

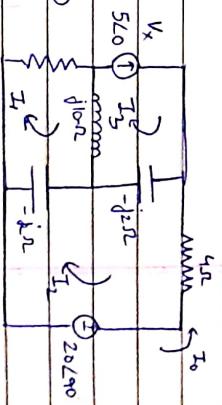

$$M_1 \rightarrow -8I_1 - j_{10}(I_1 - I_3) - (j2)(I_1 - I_2) = 0$$

$$M_2 \rightarrow (-j2)(I_2 - I_1) - (-j2)(I_2 - I_3) - 4I_2 - 20\angle 90^\circ = 0$$

$$M_3 \rightarrow V_k - (-j2)(I_3 - I_2) - j10(I_3 - I_4) = 0 \quad I_3 = 5 \angle 0^\circ$$

$$I_0 = 6.12 \angle 144.28^\circ = -I_1$$

$$5L_0 \text{ } \left(\begin{array}{c} \text{---} \\ \text{---} \end{array} \right) \text{ ---} -j\omega$$

8a
j10

$$\text{---} -j\omega^2$$



$$I_0 = I_0' + I_0''$$

$$I_0'' = -2.647 + j1.176$$

$$= 2.89 L - 23.95^\circ$$

$$I_0 = (-2.353 + j2.353) + (-2.647 + j1.176)$$


$$= -5 + j3.529$$

$$= 6.12 L 144.78^\circ$$

② Superposition

$$\omega = 2 \rightarrow$$
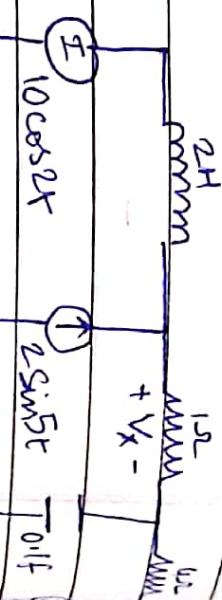
$$j4a \text{ } \left(\begin{array}{c} \text{---} \\ \text{---} \end{array} \right) \text{ ---} + V_0' -$$



a.

Q. Source Transformation

$$V_s = \text{?}$$

